



## GARISSA UNIVERSITY

UNIVERSITY EXAMINATION **2017/2018** ACADEMIC YEAR **ONE**  
**SECOND** SEMESTER EXAMINATION

SCHOOL OF EDUCATION, ARTS AND SOCIAL SCIENCES

FOR THE DEGREE OF BACHELOR OF EDUCATION (ARTS)

COURSE CODE: COM 217

COURSE TITLE:

EXAMINATION DURATION: 3 HOURS

DATE: /12/17

TIME: .00-.00 PM

---

### INSTRUCTION TO CANDIDATES

- The examination has SIX (6) questions
- Question ONE (1) is COMPULSORY
- Choose any other THREE (3) questions from the remaining FIVE (5) questions
- Use sketch diagrams to illustrate your answer whenever necessary
- Do not carry mobile phones or any other written materials in examination room
- Do not write on this paper

This paper consists of TWO (2) printed pages

*please turn over*



**QUESTION ONE (COMPULSORY)**

- (a). Differentiate between extrinsic and intrinsic semiconductor materials [2 marks ]
- (b). i. Describe the formation of a pnp semiconductor material . [2marks]  
 ii. Use the idea of free electrons to explain why semiconducting materials have higher resistivity than conducting materials. [2 marks ]
- (c). i. Define electron mobility. [1mark]  
 ii. An intrinsic semiconductor current (I) flow is due to electrons and holes

$$I = I_e + I_h = enV_eA + e\rho V_hA$$

Where e = electron charge

n= no of electrons per unit volume of conductor

$V_e$ = electron drift velocity

$V_h$ =hole drift velocity

$\rho$ =hole density

Show that resistivity,  $\rho = \frac{1}{en(\mu_e + \mu_h)}$  [3marks]

- iii. Mobilities of electrons and holes in a sample of intrinsic germanium at room temperature are  $0.36\text{m}^2/\text{v-s}$  and  $0.17\text{m}^2/\text{v-s}$  respectively. If the electron and hole densities are each equal to  $2.5 \times 10^{-19}\text{m}^3$ , Calculate germanium conductivity [ 3marks]
- (d). Sketch and explain the common-emitter static input characteristic. [3 marks]
- (e). The base of pnp bipolar transistor is grounded. A battery is connected between the emitter and the base. Another battery is connected between the base and the collector. This is known as the common base configuration.
- i. Draw the circuit indicating polarities of the batteries that would put the transistor in the forward active mode. Explain why you have chosen these polarities [5marks]
- ii. Why is the emitter more heavily doped? [2marks]
- iii. How do the carriers that are emitted into the base reach the collector. [2marks]



**QUESTION 2 (15 MARKS)**

- (a). Define fabrication and state why an npn BJT is preferred. [2marks]
- (b). Outline the process of fabrication of a BJT transistor. [6marks]
- (c). i. State two applications of diodes. [2marks]
- ii. Determine if the zener diode in the fig.1 below is properly biased, find  $I_Z$  and power dissipated by the diode. [5marks]

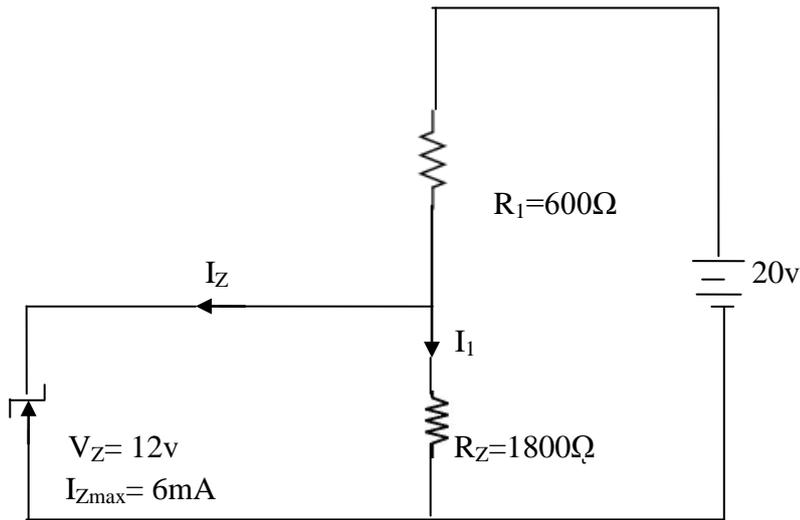


Fig.1

**QUESTION 3 (15 MARKS)**

- (a). Explain how temperature affects bias variations. [2marks]
- (b). The circuit below represents a bias connection. Use the circuit to answer questions that follow.

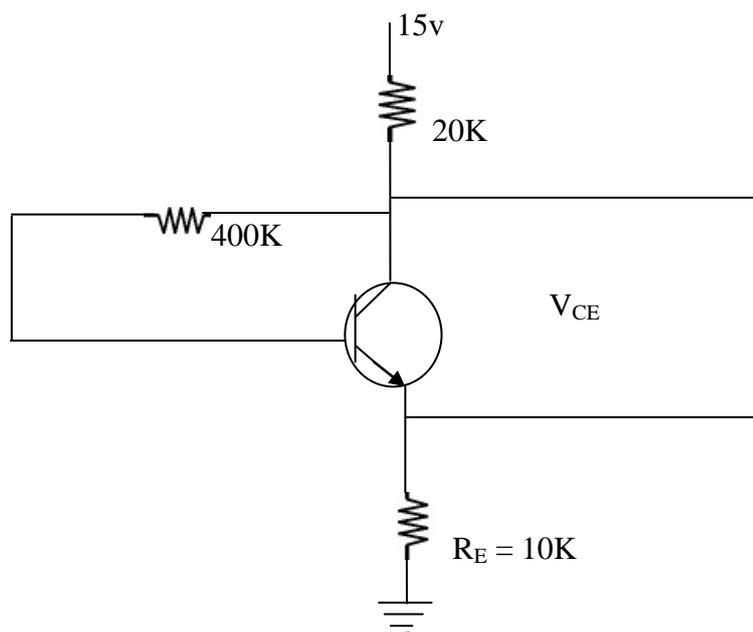


Fig.2



- i. Name the bias connection [1mark]
- ii. Find
  - a).  $I_{C(sat)}$  [2 marks]
  - b).  $V_{CE}$  [3 marks]
  - c).  $K_{\beta}$  neglect  $V_{BE}$  and take  $\beta=100$  [2marks]
- iii. Define Quiescent point [1mark]
- iv. For the circuit below draw the d.c load line and locate its Quiescent or dc working point. [4 marks]


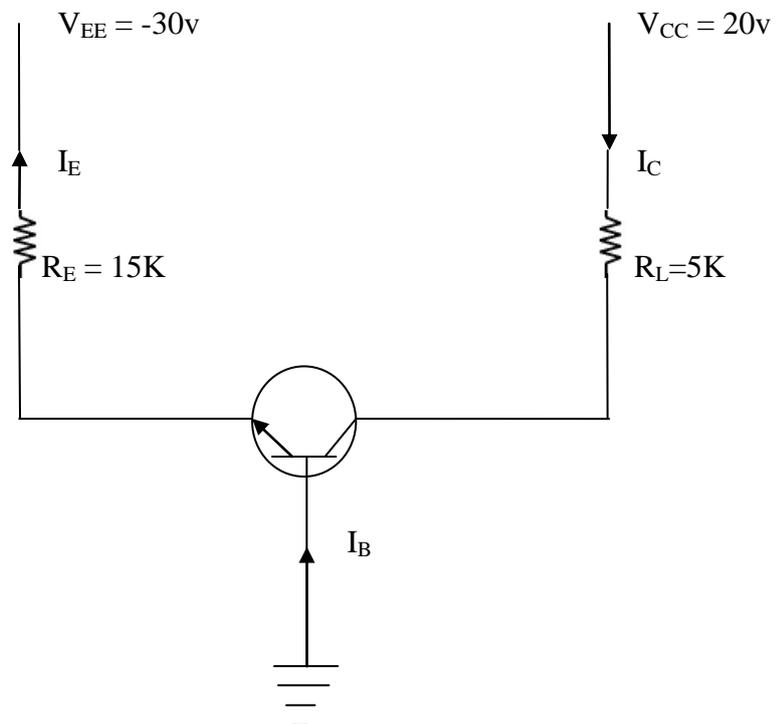


Fig.3

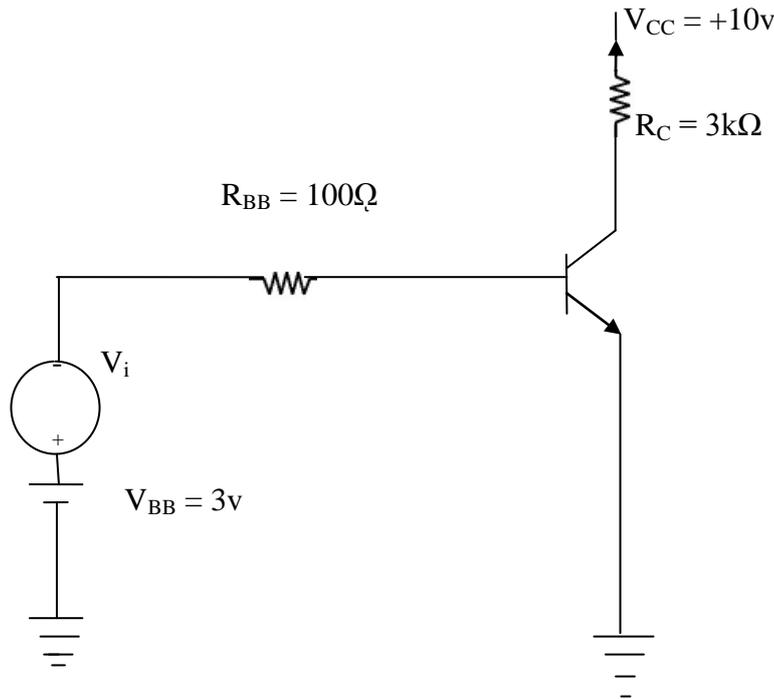

**QUESTION 4 (15 MARKS)**

- (a). State procedure for drawing ac equivalent circuits. [3marks]
- (b). Determine the small signal AC voltage gain for the circuit below assuming  $\beta=100$  and the output voltage taken at the collector terminal.



[10 marks]

Fig.4

- (c). State two equivalent active mode small signal circuit models for BJT. [2 marks]

**QUESTION 5 (15 MARKS)**

- (a) Small signal amplifiers also referred to as voltage amplifiers have three main properties. State and define these properties. [6marks]
- (b). Consider the circuit below. Calculate the voltage gain  $A_V = \frac{V_{out}}{V_{in}}$  (Room temperature value  $V_T=25mV$ ). [4 marks]



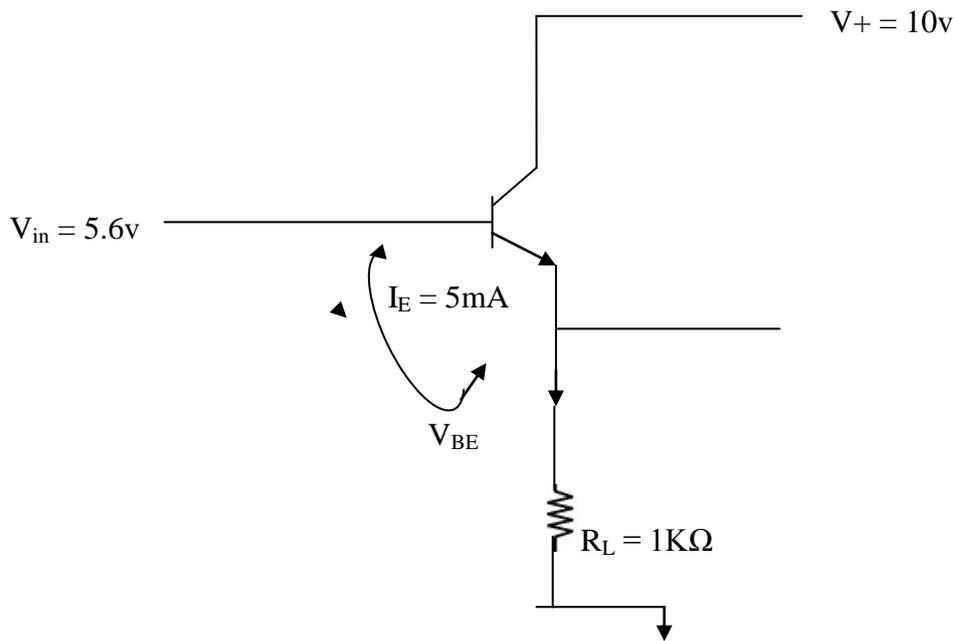


Fig. 5

- (c). i. State two applications of a UJT. [2marks]
- ii. A one phase half wave rectifier supplies power to a  $1K\Omega$  load the input supply voltage is  $200 V_{rms}$ . Neglecting forward resistance of the diode, calculate  $V_{dc}$  and ripple voltage(rms value) [3marks]

**QUESTION 6 (15 MARKS)**

- (a). State the symbol and function of a thyristor. [2 marks]
- (b). i. Briefly describe the operations of a thyristor. [3 marks]
- ii. Name two applications of silicon controlled rectifiers (SRC). [2 marks]
- (c). What is the difference between UJT and FET. [2 marks]
- (d). A given silicon UJT has an inter base resistance of  $10K$ ,  $R_B = 6K$  with  $I_E = 0$ . Find
- i. UJT current if  $V_{BB} = 20V$  and  $V_E$  is less than  $V_P$  [2 marks]
- ii. Peak point voltages,  $V_P$  [3 marks]
- (e). State the function of DIACS. [1 mark]

